

Question 1. Explain shortly the following concepts related to the dynamics of a switched-mode converter (Note: Repeating the English words does not suffice): **a)** SSA method, **b)** two-port model, **c)** state space, **d)** PI, **e)** PCM-control, and **f)** DDR-control. (á 1pt)

Question 2. Fig. 1 shows an electrical equivalent circuit representing the dynamics of a certain class of switched-mode converters. Define symbolically based on Fig. 1 **a)** Z_{o-o} , **b)** Z_{in-o} , and **c)** T_{oi-o} (Each subquestion gives 2 pts).

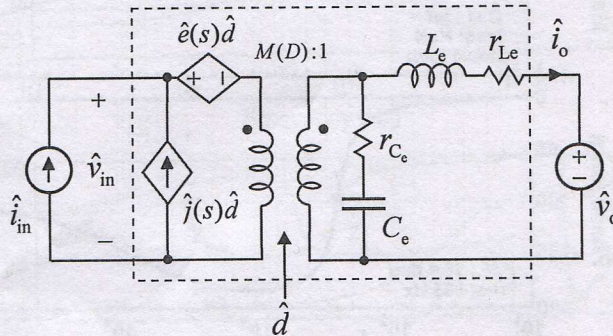


Fig. 1.

Question 3. A control-block diagram representing a generalized closed-loop input dynamics of an input-side-controlled converter is given in Fig. 2. **a)** Define the equation for the feedback-loop gain (L_{in}) using the symbols of Fig. 2, **b)** Define symbolically the closed-loop $\hat{y}_{in} / \hat{u}_{in}$, and **c)** Define symbolically $\hat{y}_{in} / \hat{u}_{r-in}$. (Each subquestion gives 2 pts)

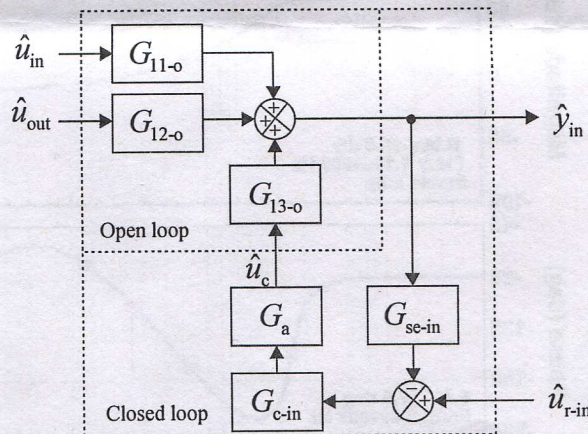


Fig. 2.

Question 4. The frequency responses of the control-to-output-voltage transfer function (G_{co-o}) and the output-voltage-feedback loop gain (L_{out}) of a buck converter are shown in Fig. 3a, and Fig. 3b, respectively.

- a) Compute the approximate value of the output capacitor of the converter when its output inductor is 400 μH ? (2pts)
- b) Evaluate the feasibility of the control design based on Fig. 3b: Why it is /Why it is not? (2pts)
- c) What is the type of the used controller? I, P, PI, PID? Justify your answer! (2pts).

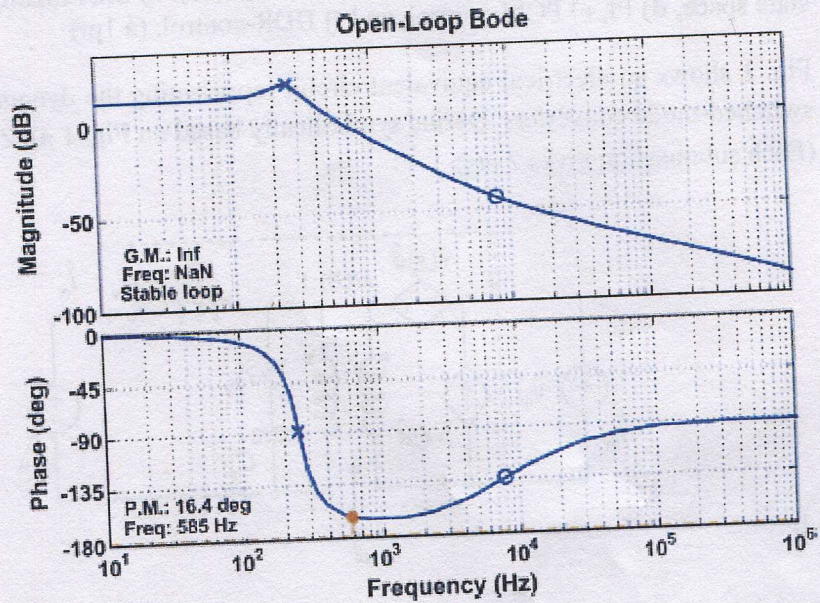


Fig. 3a.

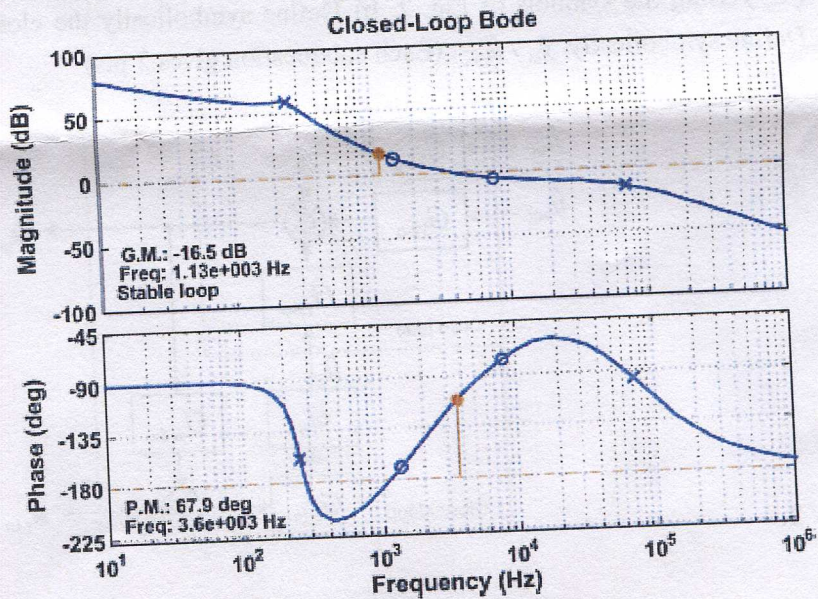


Fig. 3b.

Question 5. The measured open-loop (Z_{in-o}), closed-loop (Z_{in-c}), and short-circuit (Z_{in-sco}) input impedances of the output-voltage-feedback-controlled converter as well as the output impedance (Z_s) of the input EMI filter are given in Fig. 4. Analyze the effect of the input filter on a) the stability of the converter, b) load-transient responses, and c) voltage-loop gain. Without the input filter, the converter is stable and the transient performance is excellent. Justify your thoughts based on Fig. 4 and the underlying formulas. The value of each sub-question is 2 points.

$$G_{co-o}^S = \frac{1 + Z_s / Z_{in-o}}{1 + Z_s / Z_{in-c}} G_{co-o} \quad Z_{o-c}^S = \frac{1 + Z_s / Z_{in-sc}}{1 + Z_s / Z_{in-c}} Z_{o-c} \quad Y_{in-c} = \frac{Y_{in-o}}{1 + L_{out}} + \frac{L_{out}}{1 + L_{out}} Y_{in-o}$$

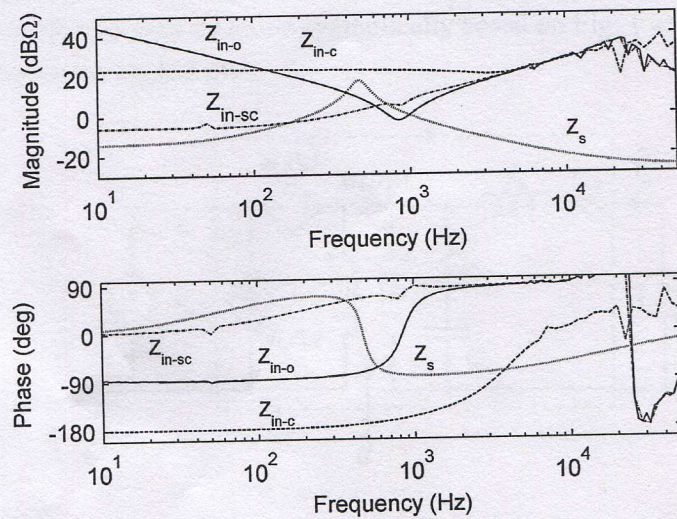


Fig. 4