

- Q1: a) Find Thevenin equivalent for the circuit shown in Figure 1. The rms voltage of the sinusoidal voltage source $V_R = 230 \angle 0^\circ$ V and frequency 50 Hz. $R_1 = 27 \Omega$, $R_2 = 8 \Omega$, $L_1 = 150$ mH, $L_2 = 60$ mH and $C = 67 \mu\text{F}$. [3 pts]

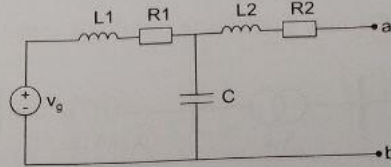


Figure 1. Electric circuit of Question 1 a).

- b) Below are presented unbalanced three-phase voltages for Phases a, b and c. Find the symmetrical components for the voltage of Phase a. Draw the phasor diagram which includes the original phasor V_a and its symmetrical components. [3 pts]

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1.1 \angle 9^\circ \\ 0.8 \angle 130^\circ \\ 1.2 \angle -70^\circ \end{bmatrix} \text{ p.u.}$$

- Q2: Three-phase synchronous generator has a rated power 25 MVA and a rated voltage 11 kV. It has a synchronous reactance of 1.2Ω . The generator is feeding full load 25 MVA (1 pu) at 0.9 power factor lagging at rated voltage. Calculate the excitation emf (E_f) and power angle δ , when
- power factor is 0.9 lagging [2 pts]
 - power factor is 0.9 leading [2 pts]
 - Calculate reactive power drawn by the load with power factor 0.9 lagging. [2 pts]

- Q3: The electric circuit in Figure 3 comprises three nodes in addition to the reference node 0 (ground), two voltage sources, 5 reactive branches, one of which is capacitive, connected as shown in Figure 3. All the relevant parameter values are given on the figure (2pts/sub-question).
- Determine the nodal admittance matrix of the electric circuit.
 - Calculate the voltage at Node 2.
 - Determine the real (P) and reactive (Q) powers injected by two voltage sources at Nodes 1 and 3.

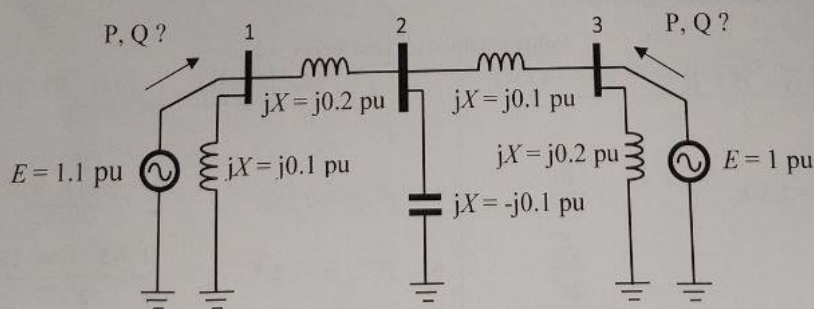


Figure 3. The electric circuit of Question 3.

- Q4:** The one-line diagram shown in Figure 3 represents a three-phase power network, for which per-unit values of positive, negative and zero sequence parameters, are available (2 pts/sub-question).
- Draw the sequence networks and determine the positive-sequence (1), negative-sequence (2) and zero-sequence (0) Thevenin impedances, as seen from node 4.
 - Calculate the fault current when three phase short-circuit occurs at Node 3. Fault impedance $Z_f = 0.1 \text{ pu}$.
 - Calculate the fault current when single line-to-ground fault occurs at Node 4. Fault impedance $Z_f = 0.1 \Omega$.

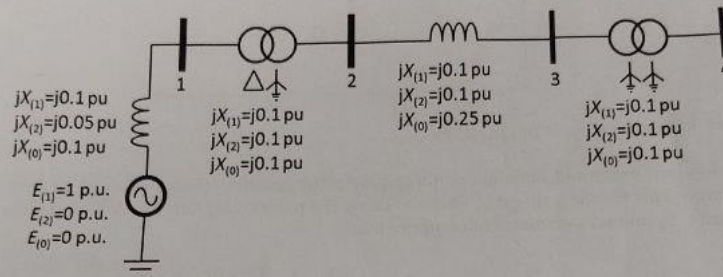


Figure 3. The electric circuit of Question 4.

- Q5:** Figure 4 presents a first order RC circuit. A step change of 10 V is applied to the input voltage u_{in} . Initial conditions are zero, i.e. i_{in} and u_o are zero.

- Determine transfer functions for determining u_o and i_{in} . [3 pts]
- Apply Laplace transform and determine the responses for u_o and i_{in} in a time domain. Utilize the table of Laplace Transforms below. The mathematical expressions as a function of time are acceptable, the graphs are not required. [3 pts]

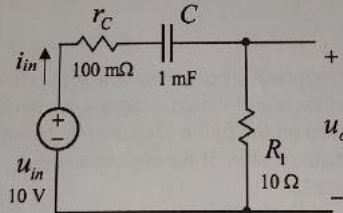


Figure 4. RC circuit of Question 5.

Table of Laplace Transforms

$f(t) = \mathcal{L}^{-1}\{F(s)\}$	$F(s) = \mathcal{L}\{f(t)\}$	$f(t) = \mathcal{L}^{-1}\{F(s)\}$	$F(s) = \mathcal{L}\{f(t)\}$
1. 1	$\frac{1}{s}$	2. e^{at}	$\frac{1}{s-a}$
3. $t^n, n=1,2,3,\dots$	$\frac{n!}{s^{n+1}}$	4. $t^p, p > -1$	$\frac{\Gamma(p+1)}{s^{p+1}}$
5. \sqrt{t}	$\frac{\sqrt{\pi}}{2s^{\frac{3}{2}}}$	6. $t^{n-\frac{1}{2}}, n=1,2,3,\dots$	$\frac{1 \cdot 3 \cdot 5 \dots (2n-1)\sqrt{\pi}}{2^n s^{n+\frac{1}{2}}}$
7. $\sin(at)$	$\frac{a}{s^2+a^2}$	8. $\cos(at)$	$\frac{s}{s^2+a^2}$